

Total No. of Questions-8]

[Total No. of Printed Pages-4

B.E. III Semester Examination**BE - III/12(A)****233274****IT. ENGG.****No.: ECE - 313****Electronics)***Time Allowed- 3Hou**Maximum Marks-100*

Note:- Attempt $\frac{1}{2}$ e questions in **all** by selecting atleast **One** question from each unit. All questions carry **equal** marks.

Unit - I

1. a) (1) Discuss Diode capacitance and static resistance of Diode. Explain dynamic resistance & derive for the same (10)
- b) (1) Explain the Tunnel Diode & Schottky diode. Draw symbol & characteristics (10)

OR


2. a) (1) Explain with neat diagram the working of capacitor filter & derive an expression for ripple factor with necessary waveform. (15)
- b) (1) For a Ge diode having reverse current of 1μ Amp. Calculate the dynamic r_f and r_r at a voltage of $10.25V$ applied across diode. Assume $V_T = 26$ mv. — (5)

Unit - II

3. a) Explain the working of Transistor as C.B. configuration. Draw the I/P and O/P characteristics & show active, saturation and cutoff regions. How the characteristics can be modified by Early effect? (10)

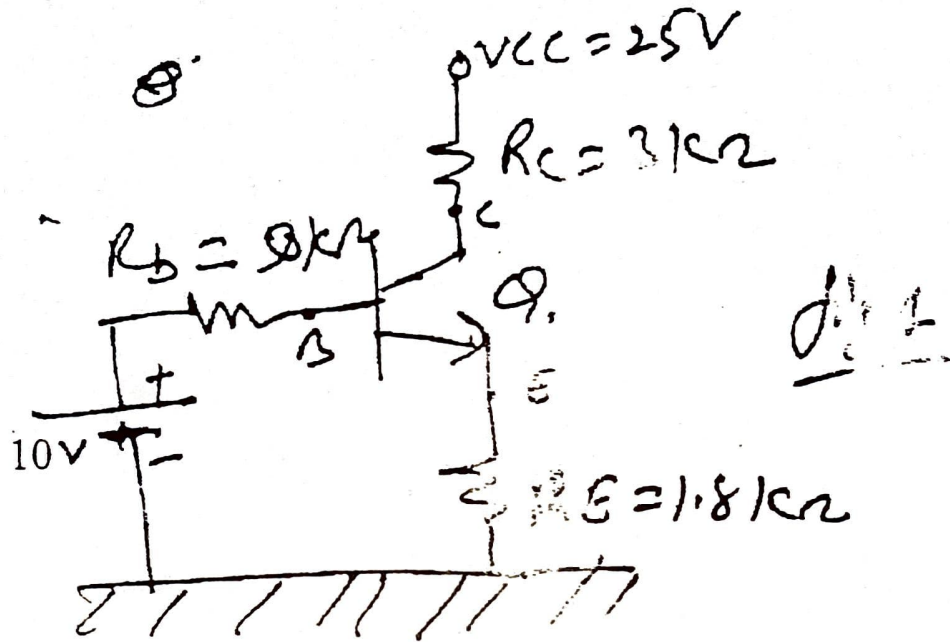- b) The silicon Transistor shown in Fig.1 has following characteristics.

$\beta = 100, V_{CE sat} = 0.2V, V_{BE sat} = 0.8V, V_{BE active} = 0.7V,$
 $V_{BE cut in} = 0.5V$ and $V_{BE cut off} = 0V$. Determine the state
 in which the transistor is (10)



OR

4. a) Derive an expression for S, S' and S'' of voltage divider Bias. (10)
- b) A GE transistor is used for self bias configuration with $V_{cc} = 16V, R_c = 1.5k\Omega$ and The operating Pts. are $V_{ce} = 8V$ and $I_c = \dots$ Amp. If $S = 10$, calculate, values of R_1, R_2 and R_E of circuit (10)

Unit - III

5. a) Discuss the JFET parameters and their relations. Also compare JFET, JFET and MOSFET (10)
- b) Explain the working of MOSFET in Enhancement mode. Draw the symbol, characteristics. (10)

OR

6. a) Derive an Expression for A_v , R_i , R_o in Case of JFET in C.D. amplifier as small signal mode with & without R_D . (10)
- b) Fig.2. Shows the JFET amplifier circuit. If the JFET has $I_{DSS} = 3mA$, $V_p = -2.4V$ and $r_d \gg R_d$. Calculate I_{DS} , V_{DS} and V_{as} . Also calculate A_v , R_i , R_o .

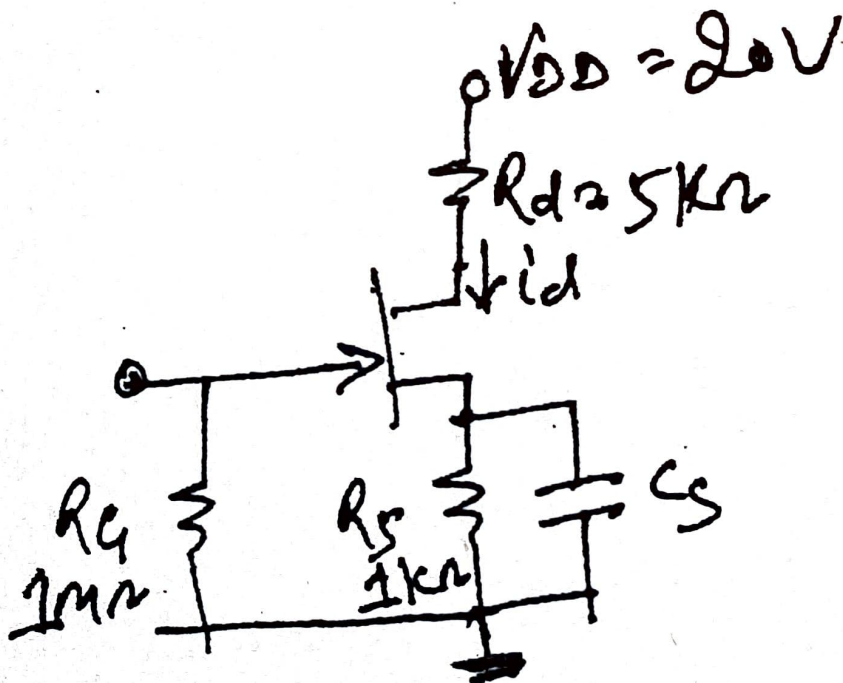


Fig 2.

(10)

2004/4

Unit - III

5. a) Discuss the JFET parameters and their relations. Also compare BJT, JFET and MOSFET (10)
- b) Explain the working of MOSFET in Enhancement mode. Draw the symbol, characteristics. (10)

OR

6. a) Derive an Expression for A_v , R_i , R_o in Case of JFET in C.D. amplifier as small signal mode with & without R_D . (10)
- b) Fig.2. Shows the JFET amplifier circuit. If the JFET has $I_{DSS} = 3mA$, $V_p = -2.4V$ and $r_d \gg R_d$. Calculate I_{DS} , V_{DS} and V_{as} . Also calculate A_v , R_i , R_o .

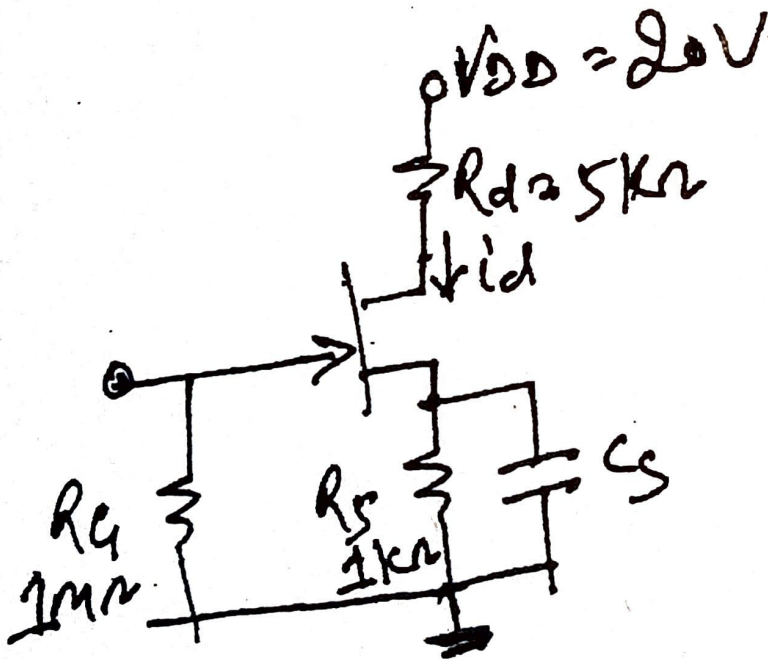


Fig 2.

(10)

[Turn Over]

2004/14

Unit - IV

7. Explain with neat diagram, the working of Op - Amp as clipper and clamper. Draw the I/P and O/P waveforms (20)

OR

8. Explain with neat diagram, the working of Op - Amp as square wave, Triangular wave & Saw tooth wave Generator. Derive the Expression for the same (20)

