

Total No. of Questions-8]

[Total No. of Printed Pages-4

B.E. III Semester Examination

BE - III/6(B)

214485

IT. ENGG

Course No.: ECE - 313

(Basic Electronics)


Time Allowed- 3 Hours

Maximum Marks-100

Note : Attempt any five questions in all by selecting atleast one question from each Unit . All questions carry equal marks.

Unit - I

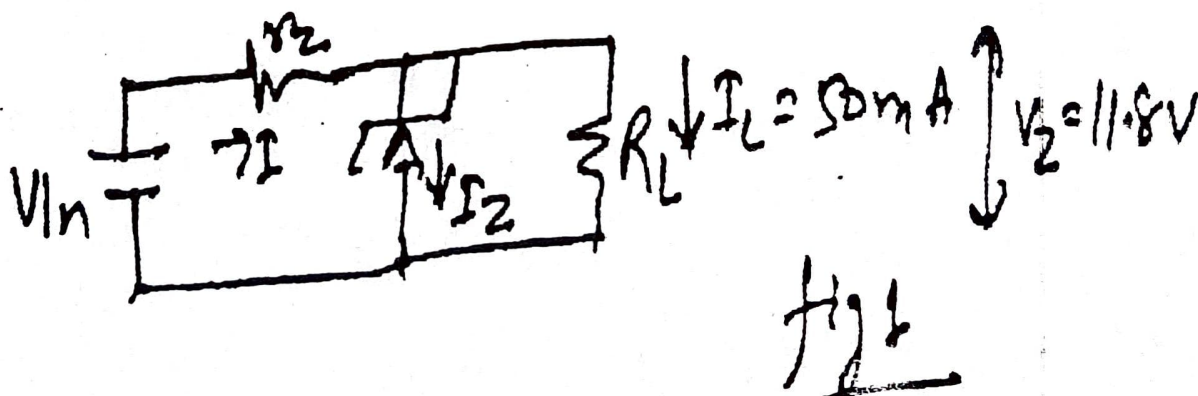1. a) ① Draw & Explain the working of P-N-diode, its Equivalent circuit, V-I characteristics & Temperature effect on V-I characteristics with Equation. 12
- b) ① Estimate the value of Zener series resistor if $V_z = 11.8V$
 $P_z = 400 \text{ mw}$ and $V_{in} = 17v$ to $19.5v$ State assumptions if any. It is shown in fig 1. 8



OR

2. a) Explain the working of Full wave rectifier using centre tap transformer & derive an Expression for I_{avg} , I_{rms} , V_{avg} , V_{rms} , power, η , r.f., T.U.F. 20

Unit - II

3. a) Explain with neat diagram, the working of Transistor in biased and unbiased condition. Also derive Generalized Transistor Equation. 10
- b) Draw & Explain the common Base configuration. show I/P & O/P characteristics with active, Saturation and cutoff region. How early effect affects the characteristics? 10

OR

4. a) Explain the need for stabilization. Explain the different Bias compensation Techniques. 10
- b) A Ge transistor having $h_{FE} = 50$ is to be used as an amplifier with $V_{cc} = 12V$ & $R_c = 2k\Omega$. Select suitable operating point, determine bias resistance (R_B) & Stability factor (S) for:-
- i) Fixed Bias
 - ii) Collector to Base bias
 - iii) Voltage divider bias with RE


Unit - III

5. a) Explain with neat diagram the characteristics of JFET. Also draw & derive for Transfer characteristics of JFET 10
- b) A C.S. FET amplifier with R_s unbypassed has the following circuit parameters. 10

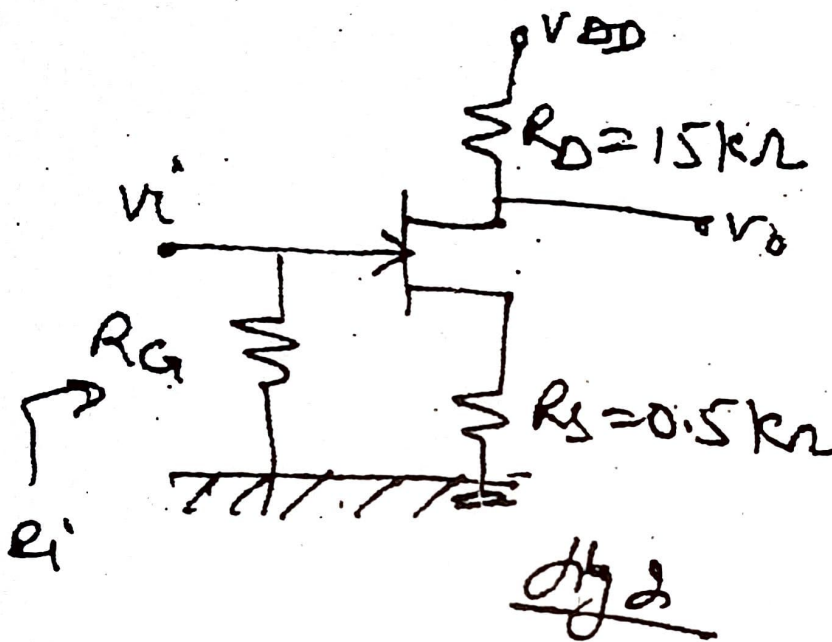(3)

BE - III/6(B) - 214485

$R_d = 15K\Omega, R_s = 0.5K\Omega, R_g = 1m\Omega, r_d = 5K\Omega, g_m = 5mS, V_{DD} = 20V$. Calculate A_v, R_i, R_o . It is shown in fig 2



2005

OR

6. a) Explain with diagram, characteristics & symbol, the working of MOSFET in Enhancement mode 10
- b) Draw the low frequency model of JFET in common source configuration with R_s and derive an Expression for drain current (i_d), A_v, R_i, R_o with & without R_s . 10

Unit - IV

7. a) Explain with neat diagram, derive the Expression for slew rate and CMRR. 10

[Turn Over]

(4)

BE - III/6(B) - 214485

- b) Derive an Expression AV_{fo} , R_{ip} , R_{op} , f_p , V_{oot} in case of voltage shunt feedback amplifier using op-amp. 10

OR

8. a) Explain Instrumentation amplifier and derive an Expression for output voltage 10
- b) Explain notch filter and all pass filter with waveform 10

