

B.E. III Semester Examination

BE(LE)-III/02(A)

25086

IT. ENGG.

Course No. ECE - 313

(Analog Electronics)

Time Allowed-3Hours


Maximum Marks-100

Note : Attempt any **five** questions in all by selecting at **two** questions from each **section**. All questions carry **equal** marks.

SECTION - I

1. a) Explain with neat diagram the working of zener diode. Draw its characteristics and show breakdown phenomenon. Explain types of breakdown phenomenon in zener diodes and derive an expression for current limiting resistor in zener diodes. (15)
- b) For silicon diode with reverse current of $0.2 \mu A$, calculate the dynamic forward and reverse resistance at a voltage of 0.72V and -0.72V applied across the diode at a room temperature of 27°C. (5)
2. a) Draw and discuss the transistor in C.E. Configuration with I/P and O/P characteristics. Derive an expression for collector current. (10)

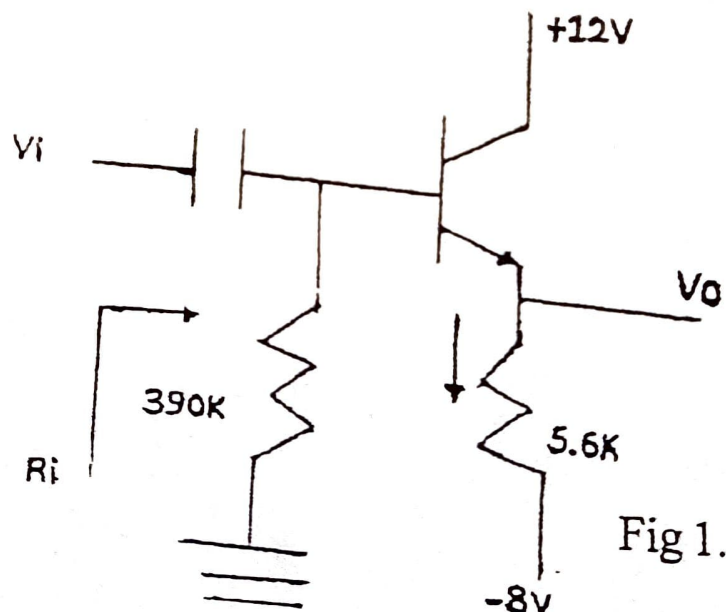- b) Design a voltage divider circuit for specified conditions:-
 $V_{cc} = 12V$, $V_{ce} = 6V$, $I_c = 1mA$, $S = 20$, $\beta = 100$,
 $V_e = 1V$. Draw the fig and find DC load line. (10)
3. a) Explain N stage cascaded amplifier, find its gain in db. (5)
- b) Draw the generalized hybrid model for a transistor. Also draw the models for CB, CE and CC configurations. Write the i/p and o/p equations. Derive the necessary equations for A_v , A_i , R_i , R_o , A_{vs} , A_{is} by taking CC transistor configuration with source resistance R_s . (15)
4. a) Draw the half wave rectifier circuit and derive an expression for all the parameters. (10)
- b) The amplifier shown in fig.1 has $h_{fe} = 100$, $h_{ie} = 3.37k\Omega$. Calculate R_i , $A_v = v_o/v_i$, $A_i = I_o/I_i$ (10)



SECTION - II

5. a) Discuss JFET parameters, find their values from the JFET characteristics. (10)
- b) Derive an expression for i_d and V_{ds} in case of fixed bias circuit. Draw the load line. (10)
6. a) Explain with neat diagram the working of Enhanced MOSFET with characteristics Symbol, transfer characteristics. (10)
- b) A common drain amplifier as shown in fig2 has following components values:- $R_1 = 2.7M\Omega$, $R_2 = 820K\Omega$, $R_s = 4.7K\Omega$, $R_L = 33K\Omega$, $g_m = 6000\mu S$, $r_d = 70K\Omega$. Calculate R_i , R_o , A_v . (10)

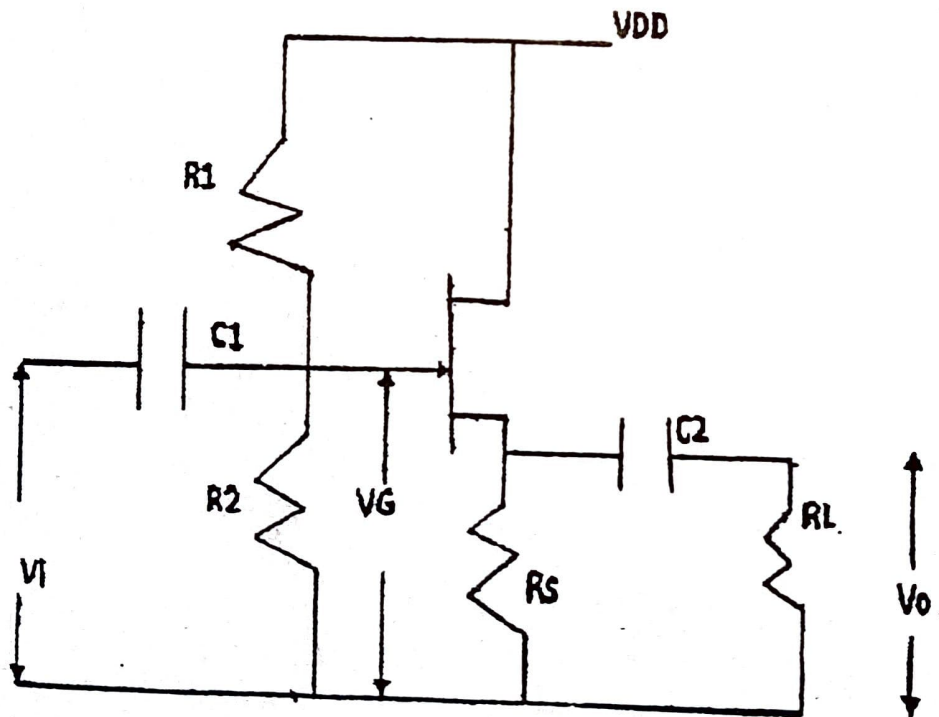


Fig. 2

[Turn Over]

2006

7. a) Explain with neat diagram and wave form the working of op-amp as AC amplifier with single power supply. (1)
- b) Explain with neat diagram the working of op-amp as band pass filter. Draw its waveform. (1)
8. Write short notes on :-
- i) D/A convertor using Binary weighted resistors (1)
- ii) Differential amplifier using two op-amps. (1)
-